

**Subject** : Electrical-network analysis


**Question** : Equation of current for an RC CIRCUIT when it is supplied by a DC source

**Answer** :

**Transient response in RC series circuit having D.C. excitation**

Let a d.c. voltage  $V$  be applied (at  $t = 0$ ) by closing a switch 's' in a series R-C circuit. The current at  $t > 0$  being 'i', application of KVL leads to

$$Ri + \frac{1}{C} \int i dt = V \quad \dots(1)$$

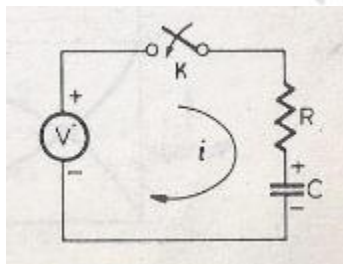

**Fig.1 Series RC circuit**

Differentiation of equation (1) results,

$$R \frac{di}{dt} + \frac{i}{C} = 0 \text{ or } \left( p + \frac{1}{RC} \right) i = 0 \quad \dots(2)$$

Equation (2) is a homogeneous differential equation whose solution will contain only complementary function, the particular function being zero.

$$\therefore i = i_C = K e^{-t/RC} \quad \dots(3)$$

With application of voltage and assuming no initial charge across the capacitor, the capacitor will not produce any voltage across it but acts as a short circuit causing the circuit current to be  $(V/R)$ .

i.e., at  $t = 0^+, i(0^+) = \frac{V}{R}$

Hence, from equation (3), at  $t = 0^+$

$$\frac{V}{R} = K$$

Finally, we obtain,  $i = \frac{V}{R} e^{-t/RC} \text{ A}$  ... (4)


It may be observed that the charging current is a decaying function. The plot is as shown in Fig. 2. As the capacitor is getting charged, the charging current dies out.

The corresponding voltage drops across the resistor and the capacitor can be obtained as follows:

$$v_R = iR = V e^{-t/RC} \quad \dots (5)$$

and 
$$v_C = \frac{1}{C} \int i dt = \frac{1}{C} \int \frac{V}{R} e^{-t/RC}$$
  


$$= V(1 - e^{-t/RC}) \quad \dots (6)$$

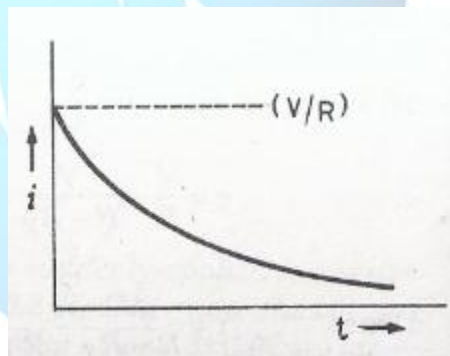

**Fig.2, Profile of current in RC charging circuit**

Observing equations (5) and (6) reveals that  $v_R$  is a decaying function while  $v_C$

is an exponentially rising function (profiles of  $v_R$  and  $v_C$  are shown in Fig3). The steady state voltage across capacitor is  $V$  volts.

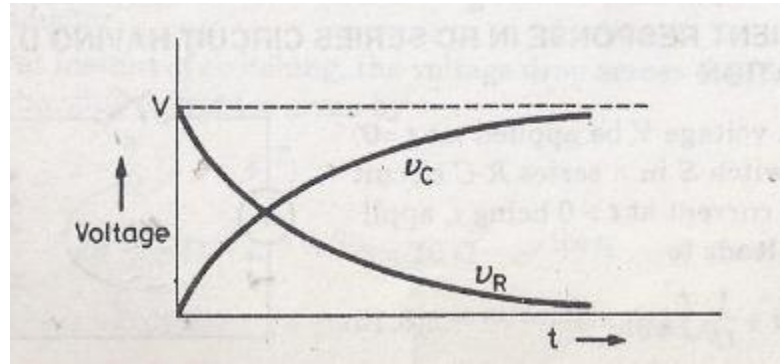

**Fig.3. Profile of  $v_R$  and  $v_C$  in RC charging circuit**